CDS1114

Introduction to Digital Systems

Latches & Flip-flops I



Lecture outcome


- By the end of today's lecture you should know
 - how basic gates combine to form latches
 - the operation of basic S-R, gated S-R and D latch
 - learn the difference between active HIGH and active LOW latches
 - identify the states of any latch and invalid con

Latches


- A latch is a temporary storage device that has two stable states SET and RESET
 - Sometimes called bistable logic device or multivibrator
- 50 They retain their states indefinitely until certain conditions change them
- Similar to flip-flops (to be covered later), latches reside in either of two states using a feedback style arrangement in which outputs are fedback to opposite inputs
- Latches begin the study of sequential logic which will later cummulate with counters and shift registers

Set-Reset (S-R) Latch

 
- Make the state of Services and the formed depending on the gates used
 - using two cross-coupled NOR gates the latch responds to active-HIGH inputs
 - using two cross-coupled NAND gates responds to active-LOW inputs



(a) Active-HIGH input S-R latch

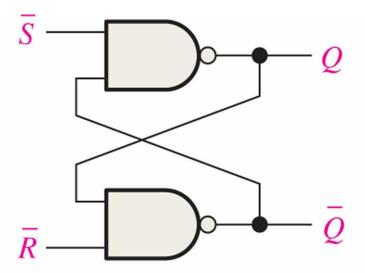

 (b) Active-LOW input \$\overline{S}\$-\$\overline{R}\$ latch




(a) Active-HIGH input S-R latch

 (b) Active-LOW input S-R latch


Active-LOW S'-R' Latch

- Two NAND gates are cross-coupled so that the output of G1 is connected to one of the inputs of G2, and vice versa
- There are two latch inputs
 - the SET input is the input that sets Q to the 1 state.
 - The CLEAR input is the input that resets Q to the O state
- 50 The gate outputs, labeled Q and Q', respectively, are latch outputs.
- Under normal conditions, the outputs will always be the inverse of each other




Active-LOW S'-R' Latch

 An alternative to using two NAND gates is to use two negative-OR gates (this is the example shown in the textbook)



S'-R' latch — resting state

 n a resting/stable state, the inputs S' and R' are normally in HIGH state



- Assuming that Q=0 (and thus Q'=1), inputs to G2 are 0 and 1 which produce Q'=1 (because NAND) so Q' remains high
- With Q'=1, both inputs to G1 are high and produce Q=0
- Conversely, if Q=1 and Q'=0, the output would be similar but inversed with Q maintaining a high output and Q' a low
 - In effect, with both inputs S and R at high, the outputs remain unchanged from the state they are currently in


S'-R' latch — resting state

- Summary of condition SET = 1 and CLEAR =1.
 - There are two possible output states when SET and RESET = 1, which are either Q = 0 and Q' = 1 or Q = 1 and Q' = 0.
 - $_{\odot}$ The outputs are remain unchanged comparing with previous state even there is new clock pulse or new input S =1 and R =1

To change the state of the S'-R' latch, one of the inputs will be pulsed LOW whenever we want to change the latch outputs


S'-R' latch — SET state

 - In the SET state, the S input is made low (because active-LOW)
- Assuming that the current state of the latch was from resting, the following occurs



- As S is pulsed to LOW, Q will go HIGH (Q=1) and this causes both inputs to G2 to become HIGH and causes Q' to go LOW
- Thus the latch ends up with Q=1 and Q'=0

 
If prior to input S being made LOW the outputs were Q=1 and Q'=0 (i.e. the latch is already in SET state), the following occurs:



- You can see that the LOW input to G1 does not affect the output of the latch and it remains SET
- Summary of condition SET = 0 and RESET =1.
 - A LOW input on SET will always cause the latch to end up in the Q = 1 state and Q' = 0.
 - This operation is called setting the latch


S'-R' latch — RESET state

 - To switch the ALS-R latch to RESET (i.e resetting the latch), the R input is made LOW
- If the current state is SET, the following occurs



- ™ When R is LOW, both inputs to G2 now result in a HIGH output Q'=1
- Both inputs to G1 are now HIGH and result in an output Q=0 thus resetting the latch

 
If prior to input R being made LOW the outputs were Q=0 and Q'=7 (i.e. the latch is already in RESET state), the following occurs:



- As before, the LOW input to G2 does not affect the output of the latch and it remains RESET
- ∞ Summary of condition SET = 1 and RESET = 0.
 - \circ A LOW pulse on the RESET input will always cause the latch to end up in the Q = 0 state and Q' = 1.
 - This operation is called clearing or resetting the latch

S'-R' latch — invalid state

 
- When SET and RESET inputs are simultaneously made LOW, this will produce HIGH levels at both NAND output, Q = 1 and Q' = 1 and violating the complement nature of the outputs
 - This condition occurs no matter what state the latch was currently in
- This is an undesired condition because the two outputs are supposed to be inverses of each other




- When in invalid state, if both input LOWs are released (made HIGH) simultaneously both outputs will attempt to go LOW and thus propagating the invalid state.
- In reality, there is always some miniscule difference in the propagation time delay at the gates so one of the gates will dominate in its transition to the LOW (or HIGH) output state

 the slower gate will then always be forced to be complement
 - In this scenario, you can NOT predict the next state of the latch

S'-R' latch — state summary

 


 


Latch starts out RESET (Q = 0).

Latch starts out SET (Q = 1).

 (a) Two possibilities for the SET operation



 


Latch starts out SET (Q = 1).

Latch starts out RESET (Q = 0).

(b) Two possibilities for the RESET operation

$1^{\frac{\overline{S}}{2}}$ G_1 Q	Outputs do not change
	state. Latch remains SET if
$1 \frac{\bar{R}}{Q_2}$	previously SET and remains RESET if previously RESET.

HIGHS on both inputs

 


Simultaneous LOWs on both inputs

1 No change/resting 0 Q=1 and Q'=0 Q=0 and Q'=1 0 Invalid/unpredictable 0


S'-R' Latch Example

 
Assuming that Q = 0 initially, determine the output Q for the NAND S'-R' latch inputs shown below



Active HIGH S-R latch

 
- Two cross-coupled NOR gates can be used as a active HIGH S-R latch (also known as a NOR gate latch)
- The arrangement is similar to the NAND latch except the Q and Q' outputs have reversed position against the inputs (i.e. $S \rightarrow Q$) and $R \rightarrow Q$)




 

S-R latch — resting state

 
In a resting/stable state, the inputs S and R are normally in LOW state > the latch remains in whatever state it is currently in/started with



 


S-R latch — SET state

 - 50 The S-R latch moves into a SET state when the S input is made HIGH
- If the initial state was SET, the latch remains as SET




S-R latch — RESET state

 - The S-R latch moves into RESET state when the R input is made HIGH
- If the initial state was RESET, the latch remains as SET



S-R latch — invalid state

 Similar to the S'-R' latch, the S-R latch also encounters an invalid state but this time when both inputs to S and R are HIGH simultaneously




S-R latch — state summary

R	S	Q	Action
0	0	Last value	No change
0	1	1	Set
1	0	0	Reset
1	1	_	Invalid condition

Gated latch

 
- A gated latch (either S-R or S'-R') adds another input ENABLE to basically turn the latch 'on' or 'off'
- The following shows the gated S-R latch logic diagram and symbol



- № In the gated latch shown, the latch will not change until EN is HIGH (=1)
- As long as EN=1, the output is controlled by the S and R inputs


Invalid state can continue to occur when both S and R are simultaneously HIGH EN - 1set s = 0 $0 \rightarrow 0$ reset EN invalid EN

Gated S-R latch timing diagram

 


Gated D latch

- A variant of the gated latch is called the D latch
 - only has two inputs EN for enable and D for data
 - when EN and D inputs are HIGH, the latch will set
 - when EN and D inputs are LOW, the latch will reset
 - There is no invalid condition since it is not possible to set both inputs to the latch gates to HIGH simultaneously
- A simple rule for the D latch is: Q follows D when the Enable is active.

 



D latch timing diagram

 

 
Exercise

Draw the resulting Q output waveform of the latches below. Assume that Q state starts LOW



 


 Repeat the process with the inputs S and R below



 
Exercise

Using the latch shown, determine outputs Q and Q' assuming that Q starts LOW



 Exercise

For a gated D latch, the waveforms below are used at the inputs D and EN. Draw the resulting timing diagram showing the output waveform you would expect to see at Q if the latch is initially RESET



Summary

- A latch forms a temporary storage device which retains its state until it is explicitly changed by its input signal (control)
- 50 The S-R and gated S-R latch has invalid condition
- Logic symbols for all the latches covered

