

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER JULY/AUGUST 2024 (TERM ID: 2420)

CDS1114 – INTRODUCTION TO DIGITAL SYSTEMS (TC1L)

10 OCTOBER 2024
9 a.m. – 11a.m.
(2 Hours)

INSTRUCTIONS TO STUDENTS

1. This Question paper consists of 5 pages excluding Cover with 4 Questions only.
2. Answer **ALL FOUR** questions. The distribution of the marks for each question is given.
3. Please write all your answers in this Question Booklet and submit this Booklet at the end of Examination.

QUESTION 1


- a) Convert this equation to Standard SOP, then use K-Map to find the simplest SOP.

[6 Marks]

$$\overline{a(b\bar{c} + \bar{a}c)}$$

- a) Determine the Q output for the gated active-high SR-latch below. Assume that Q is initially HIGH and enable is active.

[4 Marks]

 

Continued.....

QUESTION 2

a) Proof $A + \bar{A}B = A + B$

[4 Marks]

b) Based on question 2(a), construct the truth table and the resulting logic circuit simplification.

[6 Marks]

c) Simplify the Boolean Expression:


$$\overline{AB + AC} + \bar{A}\bar{B}C$$

[5 Marks]


Continued.....

QUESTION 3

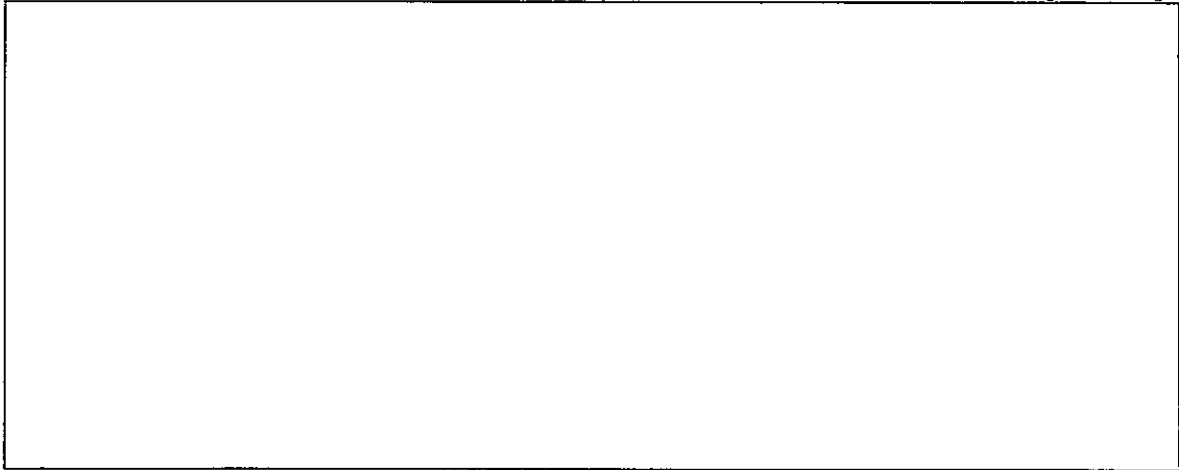
- a) Draw a circuit diagram for 3-bit asynchronous count-up counter, Q_0 for LSB, Q_2 for MSB. [3 marks]



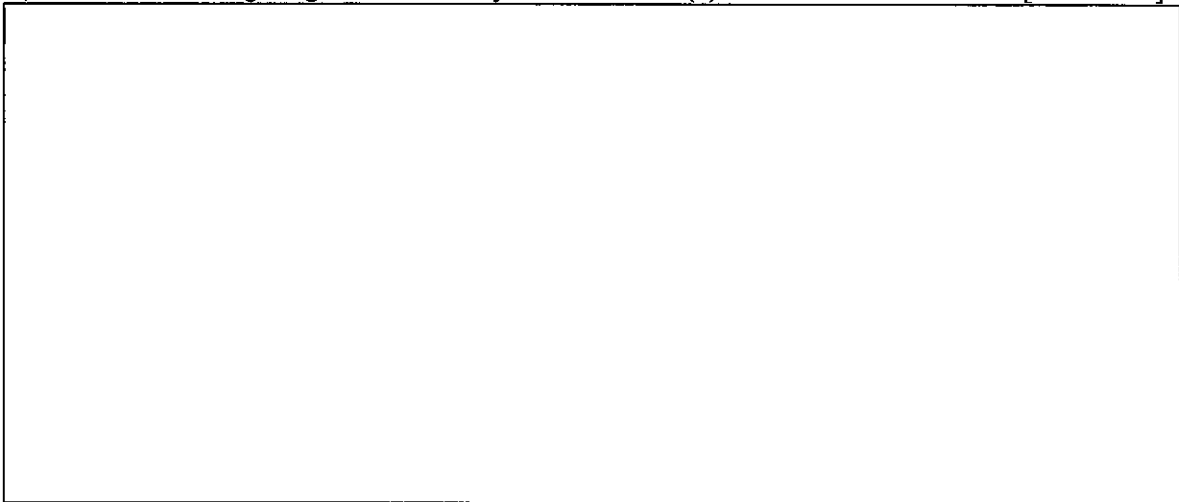- b) Draw the timing diagram based on your answer in (a). [4.5 marks]



 - c) Design a synchronous counter using JK flip-flops that follows the sequence 100,010,001, 111 and repeats. The undesired states will go to 111 on the next clock pulse **EXCEPT** for 000 and 011. 000 and 011 will go to do-not-care.
- i. Construct the state transition diagram for the above counter. [1.5 Marks]



Continued.....

- ii. Create the next state table according to the state diagram in (i) and use J-K flip-flop excitation table to define the J and K inputs for each flip-flop involved in the counter.

[3 Marks]

- iii. Perform K-map simplification for each flip-flop in the counter.

[3 Marks]

Continued.....

QUESTIONS 4

- a) Briefly explain the concept of Johnson counter. Provide an example of an application of Johnson counter. [3 Marks]

- b) Design a 4-bit Johnson counter using D flip-flops. Provide the:
- i. truth table
 - ii. circuit diagram
 - iii. sequence of states for your design. [7 Marks]

End of Page.

